

20-01-23

Lab-02

Aim: Plot output characteristics and transfer characteristics of n-mos and p-mos devices.

Apparatus: ngspice Software.

Theory:

The mosfet is actually a four-terminal device.

(i) Gate

(ii) Source

(iii) Drain

(iv) Body

* Body and Source are always short circuited to neglect body effect.

* And for n-mos $V_D > V_S$; And for p-mos $V_S > V_D$; In n-mos current flows from Drain to Source and in P-mos current flows from Source to Drain.

Transfer characteristics: The plot between V_{GS} [voltage between gate and source] and current flowing from Drain to Source (I_{DS}).


$V_{GS} - I_{DS}$

Output characteristics: The plot between V_{DS} [voltage between drain and source] and current flowing from drain to source (I_{DS}).


$V_{DS} - I_{DS}$

TO work n-mos $V_{GS} > V_{th}$ where V_{th} = threshold voltage.

TO work p-mos $V_{SG} > |V_{th}|$

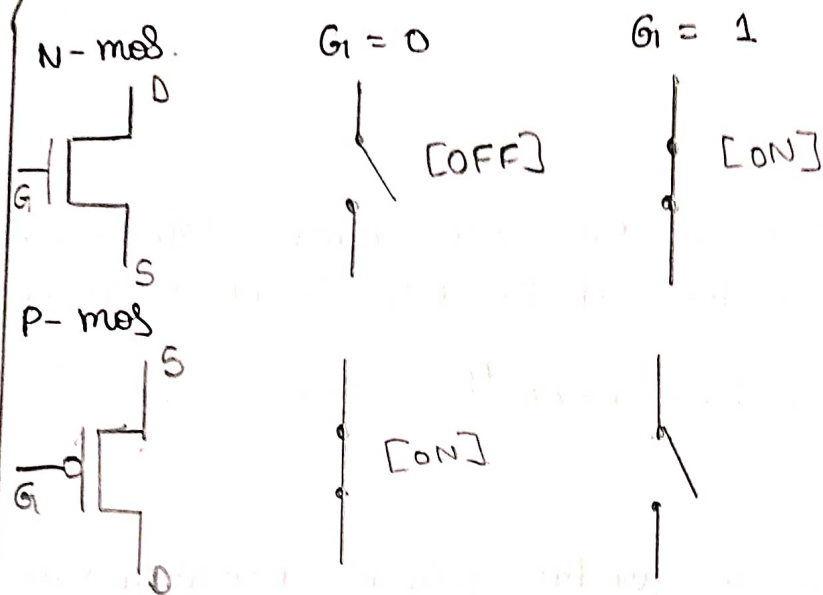

C-mos [network] :-

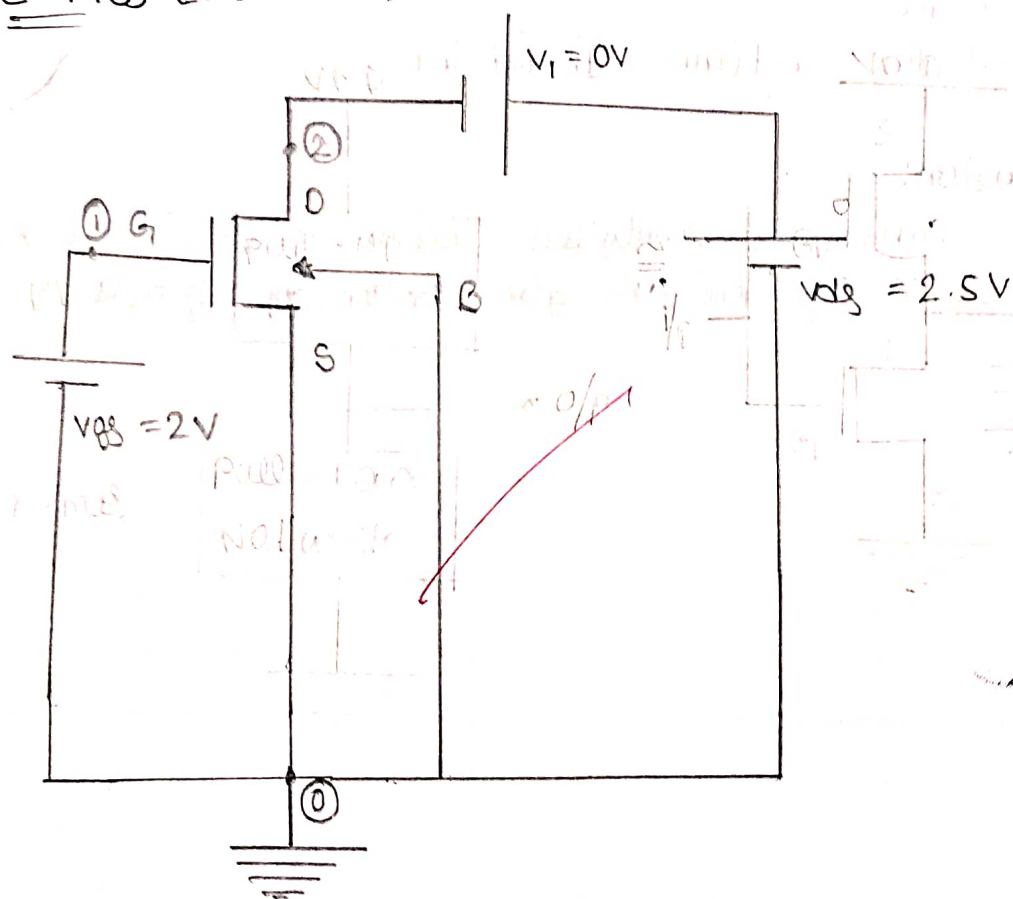

Procedure:-

- ① Name the nodes of the circuits by numbers and give "0" to ground.
- ② Make netlist by nodes. i.e. the components between which nodes like resistor, capacitor etc.
- ③ Now give the dc input for gate and check the values of Current through resistor (or) dummy voltage.
- ④ For transfer characteristics plot the graph between Gate voltage and Current through resistor.
- ⑤ For output characteristics plot the graph between Drain voltage and Current through resistor.
- ⑥ For nmos select model nmod level=54, version=4.7
- ⑦ For pmos select model pmod level=54, version=4.7
- ⑧ At device selecting always use order of D G S B respectively
D = Drain voltage (or) node number
G = Gate node number
S = Source node number
B = Body node number

For saturation mode,

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$

For Linear region

$$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

model works in only saturation mode and Linear region.

Code:-

(i) nmos

a) Transfer characteristics

Vg 1 0 2V

Vd 3 0 2.5V

V1 3 2 0V

• model nmod nmos level=54 version=4.7

m1 2 1 0 0 nmod w=100u l=10u

• dc Vg 0 2 0.1

• control

run

plot i(V1) xlabel 'Vgs' ylabel 'Id' title "V-I char of nmos"

• end c

• end.

b) output characteristics

Vg 1 0 2V

Vd 3 0 5V

V1 3 2 0V

• model nmod nmos level=54 version=4.7

m1 2 1 0 0 nmod w=100u l=10u

• dc Vdd 0 5 0.1

• control

run

plot i(Vd) ylabel 'Ids' xlabel 'Vds' title "V-I char of nmos"

• end c

• end.

(ii) p-mos

a) Transfer characteristics:

Vg 1 0 -2V

Vd 3 0 -2.5V

Vs 3 2 0V

.model pmod pmos level = 54 version = 4.7

M1 0 1 2 0 pmod w = 100u d = 10u

.dc Vg 0 -2 -0.1

.control

run

plot ~~i(V1)~~ i(V1) x label 'Vg' y label 'Id' title 'V-I char of pmos'

.endc

.end

b) output characteristics:

Vg 1 0 -2V

Vd 3 0 -2.5V

Vs 3 2 0V

.model pmod pmos level = 54 version = 4.7

M1 0 1 2 0 pmod w = 100u ; d = 10u

.dc Vd 0 -2.5 -0.1

.control

run

plot i(Vd) x label "Vd" y label 'Id' title 'V-I char of pmos'

.endc

.end.

Observations:

we observed that if we put V_{DS} as constant and V_{GS} is increased the current graph will be same, but intensity is increased.

$V_D \rightarrow$ Constant

cutoff \rightarrow saturation \rightarrow linear

$V_{GS} \rightarrow$ Constant

cutoff \rightarrow linear \rightarrow saturation

Result/conclusion:-

we have successfully plotted the V_I characteristics, output characteristics and transfer characteristics of n-mos and p-mos devices.

YJ
17/2

(A)