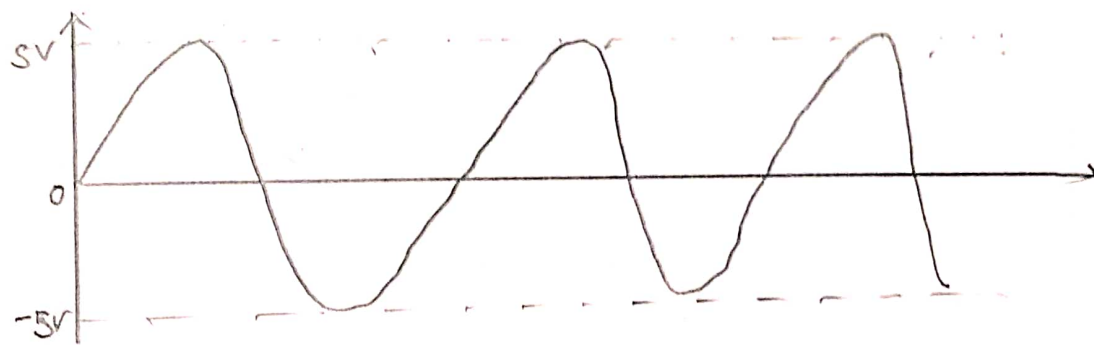



(i) DC Input.



(ii) AC Input



(iii) Transient / Pulse train

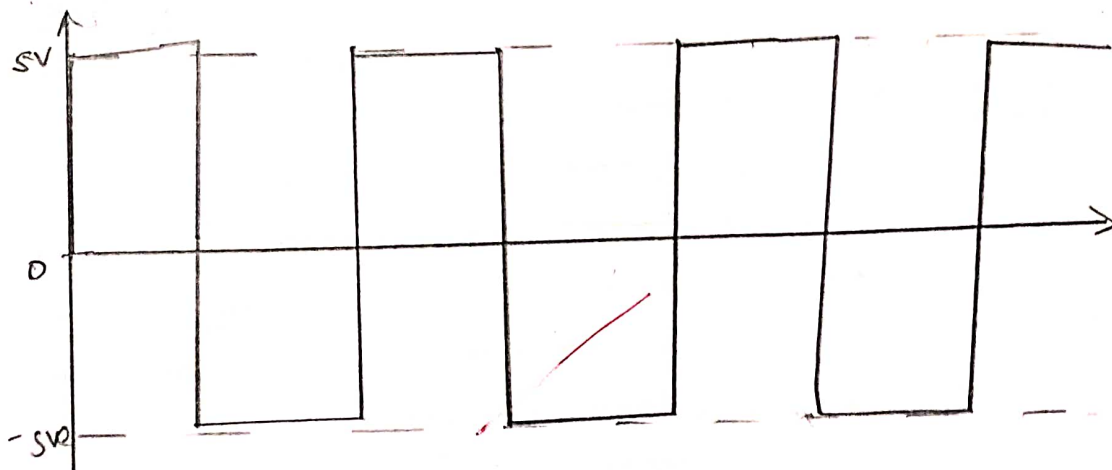

13-01-2023

Lab - 01

Aim: Analysis of voltage divider and RC Circuit on ngspice.

Apparatus :- ngspice Software

Theory:-

(i) DC Analysis:

This Analysis is used to analysis on for checking biasing conditions are set (or) not by giving dc input to circuit.

(ii) AC analysis:

This Analysis is used to check the Range (or) In a given range circuit work (or) not by giving ac input to circuit.


(iii) Transient analysis:

This Analysis is used to analysis the circuit with respect to time by giving pulses (or) pulse train as input to circuit.

Procedure

- ① Name the nodes of the circuits by 0 as Ground always.
- ② make netlist by nodes, i.e. the one (resistor) between which nodes.
- ③ Now Give the input as per AC (or) DC (or) Transient to the circuit.
- ④ Plot the Graphs between transfer (or) output character stics.

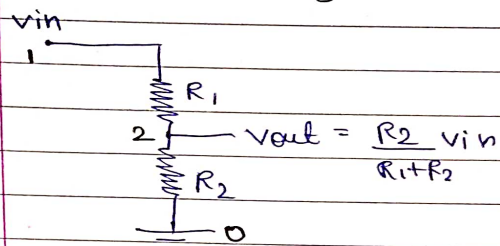Circuit - 1:- (Single R-circuit) (*) voltage divider.



Given Ground as 0

vin as 1 ; Resistor as 2
node

Code:-

1) DC-analysis

*** DC-analysis

vin 1 0 5v

R1 1 2 8k

R2 2 0 2k

• dc vin 0 5 0.1

• Control

run

Plot $V(1)$, $V(2)$ → // Plot as $V(1)$, $V(2)$

• end c

• end

voltages at

nodes 1, 2

2) AC-analysis

*** AC-analysis

vin 1 0 dc 0 ac 5

R1 1 2 8k

R2 2 0 2k

• ac dec 10 1 10k

• Control

run

• end c

• end

3) Transient analysis:

vin 1 0 pulse (0 5 0 0 0 100ms 200ms)

R1 1 2 8k

R2 2 0 2k

• tran 0.2ms 1000ms

• Control

run

Plot $V(1)$ $V(2)$


• end c

• end

// 0.2ms → width

// 1000ms → stop value

Circuit -02:- [R-C Circuit]

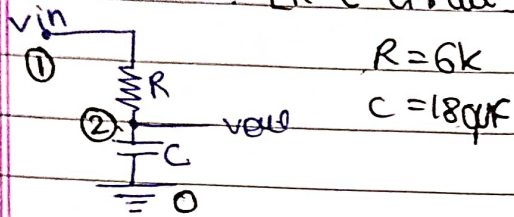

① DC-Analysis:-

*** DC Analysis

Vin 1 0 50V

R₁ 1 2 6k

C₁ 2 0 180uF

• dc Vin 0 5 0.1

• Control

run

Plot v(1), v(2).

• endc

• end.

② AC-analysis

*** AC Analysis

Vin 1 0 dc 0 ac 5V

R₁ 1 2 6k

C₁ 2 0 180uF

• ac dbc 10 1 10k

• Control

run

Plot v(1), v(2)

• endc

• end.

③ Transient analysis:-

*** Trans Analysis

Vin 1 0 pulse (0 5 0 0 0 100ms 200ms)

R₁ 1 2 6k.

C₁ 2 0 180F

• tran 0.2ms 1000ms

• measure tran time TRIG v(1) val = 0.5 Rise = 1 Tcong v(1) val = 4.5

• Control

run

Plot v(1) v(2)


• endc

• end.

Rise = 1

→ 1/f_{on}
calculating
Rise time.

Circuit - 03: (R-L-C Circuit)

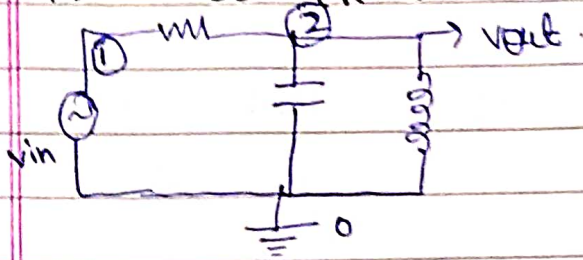

$$R = 1.2k$$

$$C = 0.1\mu F$$

$$L = 100mH$$

① DC - Analysis

*** DC Analysis

Vin 1 0 5V

R₁ 1 2 1.2k

C₁ 2 0 0.1uF

L₁ 2 0 100mH

• dc vin 0 5 0.1

• Control

run

Plot V(1) V(2)

• end c

• end

② AC - Analysis

*** AC Analysis

Vin 10 dc 0V ac 5V.

R₁ 1 2 1.2k

C₁ 2 0 0.1uF

L₁ 2 0 100mH.

• ac dc 10 1 10k

• Control

run

Plot V(1) V(2)

• end c

• end.

③ Transient analysis

*** Tran analysis

Vin 1 0 pulse (0 5 0 0 0 100ns 200ms)

R₁ 1 2 1.2k

C₁ 2 0 0.1uF

L₁ 2 0 100mH

• tran 0.2ms 100ms

• Control


run

Plot V(1) V(2)

• end c

• end

10% - 90%

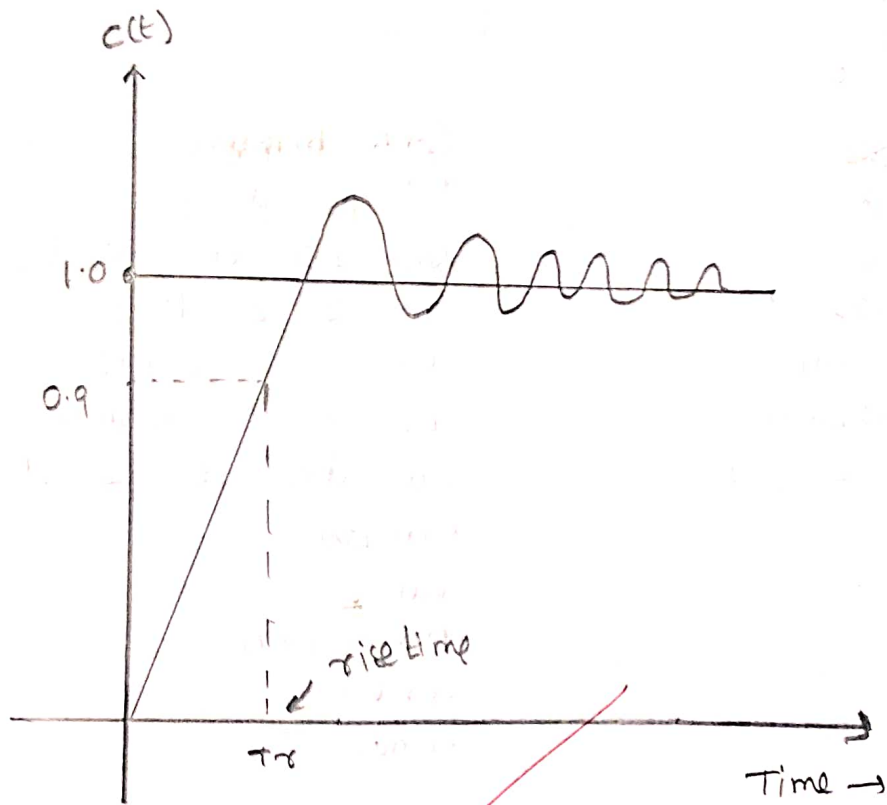

Observations:

The all plots are observed on ngspice software between v_{in} and v_{out} and also rise time of the R-C circuit is given by

$$\tau_{time} = 1.6 \times 10^{-4} \quad , \quad \tau_{avg} = 1.8 \times 10^{-4} \quad , \quad \tau_{10/90} = 2 \times 10^{-4}$$

Precautions:

- 1) Write code commands as per their original command format
- 2) For every code, first line is start with code name (e.g.)
Analysis name.
- 3) After first line continue with net-list.

Result/Conclusion:

we have successfully analyzed voltage divider in RC, RLC, R circuits on ngspice software and also plotted the graphs

A

YH
17/2